 


JUMP REGISTER (JR)

Jump register




Unconditionally jump to the instruction whose address is in register rs.

001000 (8)	jr rs	jump register	PC ← [rs]
------------	-------	---------------	-----------

- JR instruction sets the PC to the content of the register, so we have to provide a way for this data from the register file (Read data 1 port).
- a mux is needed to control whether the PC will take the value coming from the register file via the added wire or not.
- a signal has to be led from the controller to the newly added mux to control it.
- in case Jr instruction we are not need to write in register file so, we added an and gate.

Datapath modified:

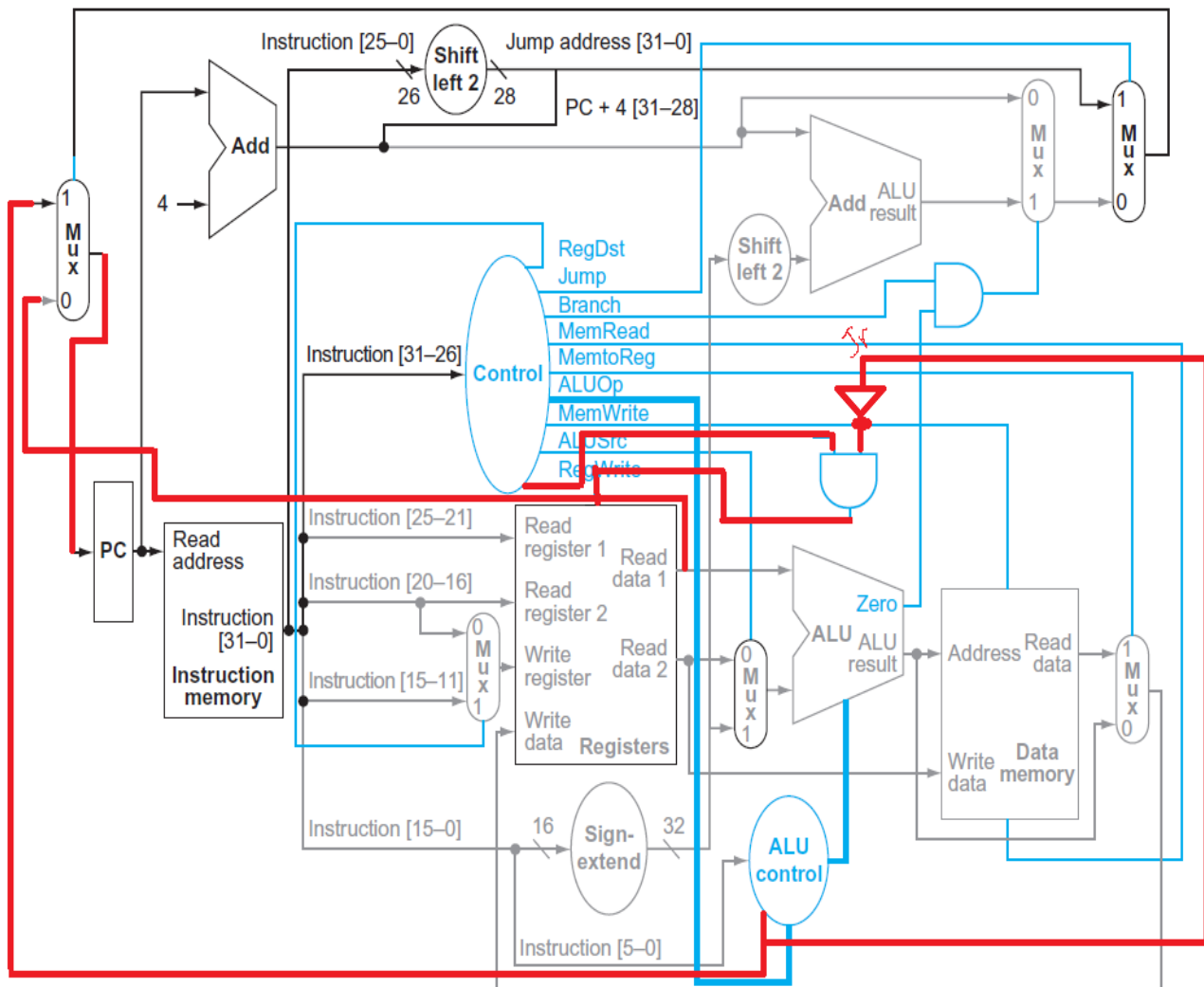

Control :

Jump	MemtoReg	MemWrite	Branch	AluControl	AluSrc	RegDst	RegWrite	Jr
0	0	0	0	00	0	1	1	1

Changes to the controller module:

```
module controller(input logic [5:0] op, funct,
                  input logic zero,
                  output logic memtoreg, memwrite,
                  output logic pcsrc, alusrc,
                  output logic regdst, regwrite,
                  output logic jump, jr,
                  output logic [2:0] alucontrol);

    logic [1:0] aluop;
    logic branch;

    maindec md(op, memtoreg, memwrite, branch,
               alusrc, regdst, regwrite, jump, aluop);

    aludec ad(funct, aluop, alucontrol);

    assign pcsrc = branch & zero;

    // implement here R-type instruction that doesn't need aluop
    always_comb
        if(op == 0) begin
            case(funct)
                6'b001000: assign {regwrite, regdst, alusrc, branch, memwrite,
                                   memtoreg, jump, aluop, jr} = 10'b0100000001;
                default: assign {regwrite, regdst, alusrc, branch, memwrite, memtoreg, jump, aluop, jr} = 10'bxxxxxxxxxx;
            endcase
        end
endmodule
```

Changes made to the datapath module:

```
// register file logic
regfile rf(clk, regwrite, instr[25:21], instr[20:16],
           writereg, result, srca, writedata);

mux2 #(5) wrmux(instr[20:16], instr[15:11],
               regdst, writereg);

mux2 #(32) resmux(aluout, readdata, memtoreg, result);
           signext se(instr[15:0], signimm);

// jr mux
mux2 #(32) jrmux(srca, pcplus4, jr, pcnext);

// ALU logic
mux2 #(32) srcbmux(writedata, signimm, alusrc, srcb);

alu alu(srca, srcb, alucontrol, aluout, zero);

endmodule
```