

# Shift Right Logical:

## introduction:

MIPS also has a **shift right logical** instruction. It moves bits to the right by a number of positions less than 32. The high-order bit gets zeros and the low-order bits are discarded.

If the bit pattern is regarded as an unsigned integer, or a positive two's comp. integer, then a right shift of one bit position performs an integer divide by two. A right shift by N positions performs an integer divide by  $2^N$ .

the following is a machine code description for Srl:

```
srl $rs $rt shift
```

## Recipe:

mux[] (multiplexer): It would select Read data 1(rs) if we're not doing a shift operation, and it would select( rt) if we are doing a shift operation.

branch Instruction: we would need to branch Instruction[10:6] (the shift amount) off of Instruction[15:0], and Instruction[10:6] would then be fed into the other port of the ALU

## implementation:

option (shift)	operation
0	output of mux[1] equals not doing a shift
1	output of mux[1] equals doing a shift operation.

## schmatic

